

---

# Switching Circuit & Logic Design

Lecture 19 :  
Programmable Logic  
Devices

---

# Programmable Logic Devices

---


- PROM – Programmable Read Only Memory
  - PLA – Programmable Logic Array
  - PAL – Programmable Array Logic
-

# Advantages

---


- Low development cost
  - Less space requirement
  - Less power requirement
  - High reliability
  - Easy circuit testing
  - Easy design modification
  - High design security
  - Less design time
  - High switching speed
-

# Read only memory

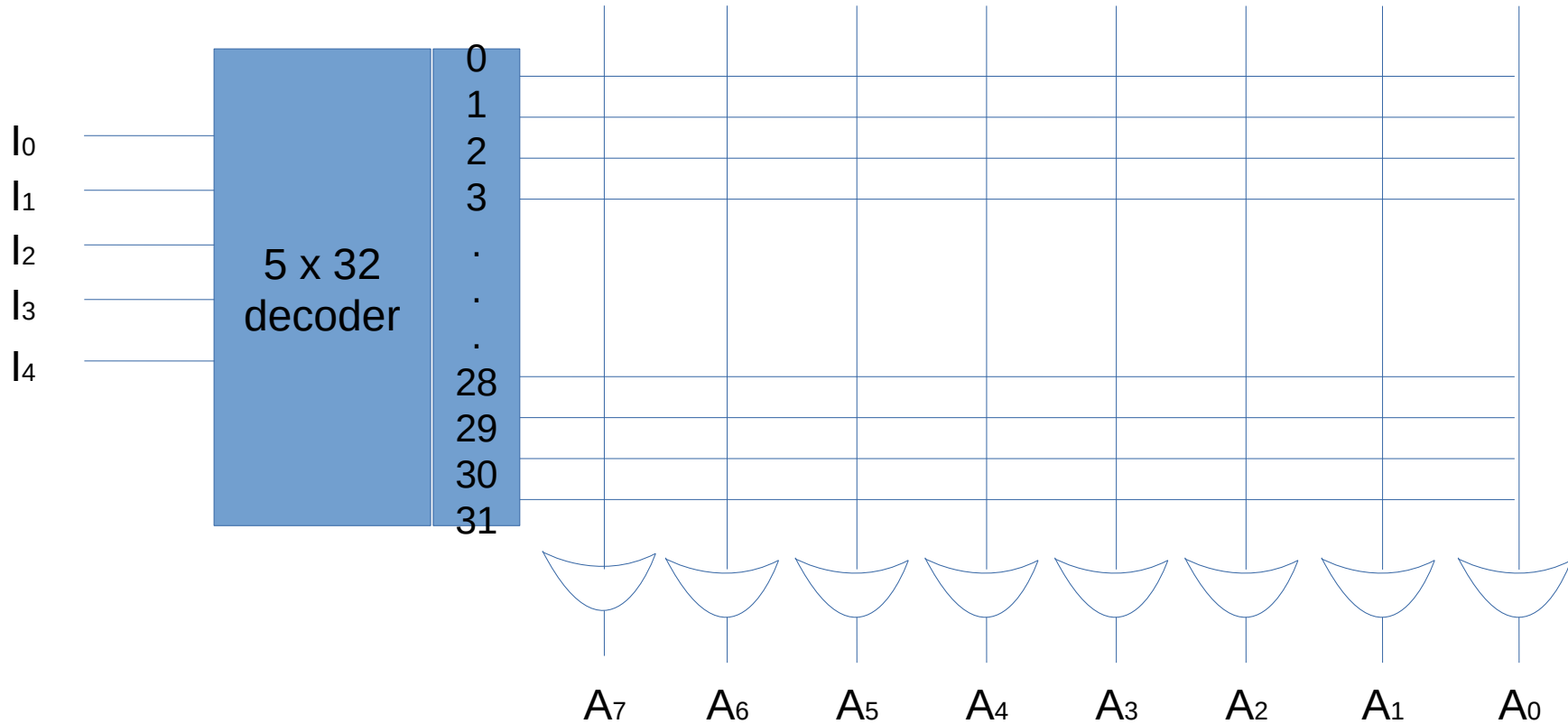

# Combinational Programmable LD

---

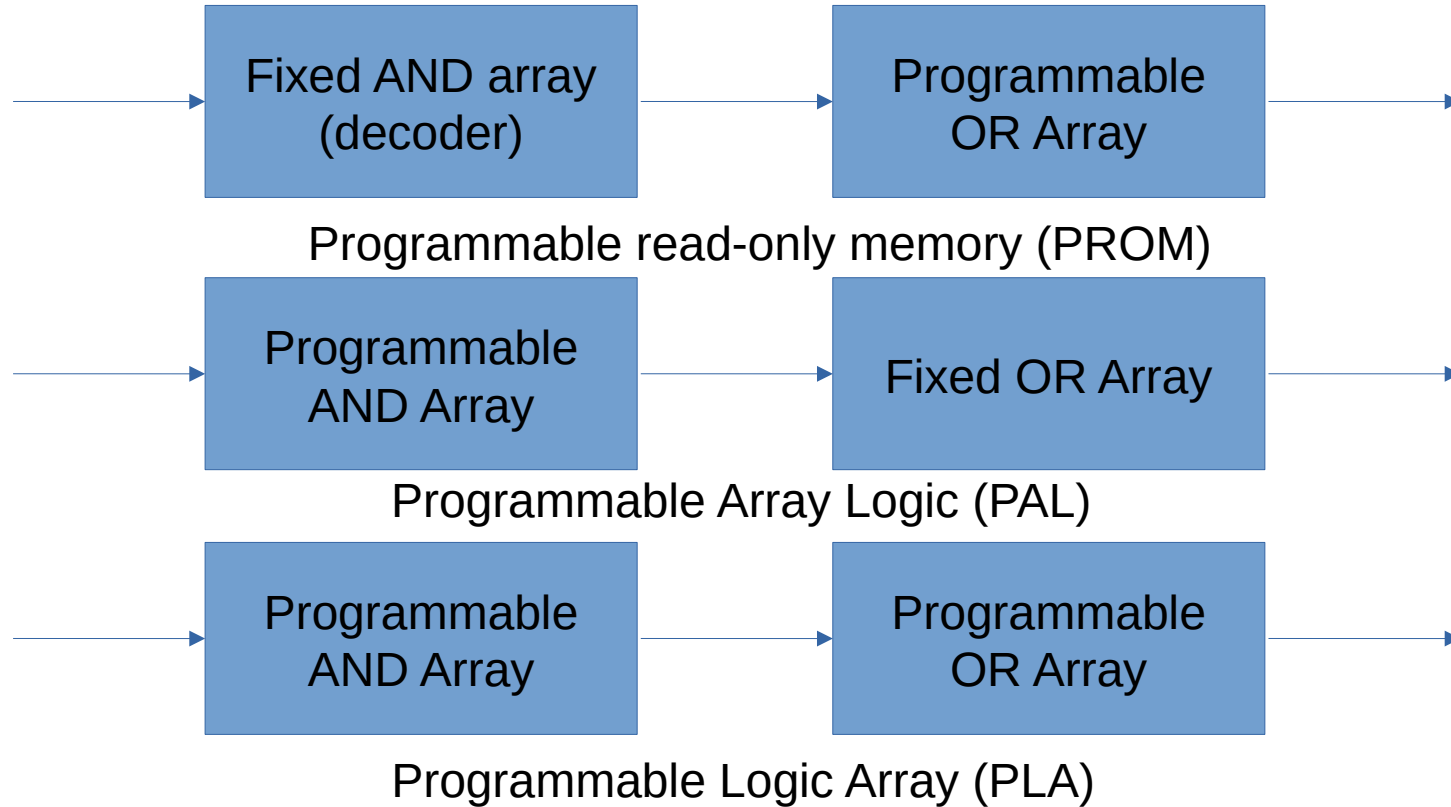

# Programmable Array Logic (PAL)

---

