

Switching Circuit & Logic Design

Lecture 24 : Counter

Types of Counters

Asynchronous Counter	Synchronous Counter
O/P of one FF to Clock of next FF	No such connection
All clocks are not simultaneous	Same clock to every FF
Simple to design	Tedious and complex
Low speed	Faster

Frequency Divider circuit

Asynchronous Counter