 


Switching Circuit & Logic Design


Lecture 1 : Introduction



Things to cover

- Digital Logic Families
- Switching theory
- Logic circuits
- Sequential Circuits
- ASM chart

Digital Logic Families



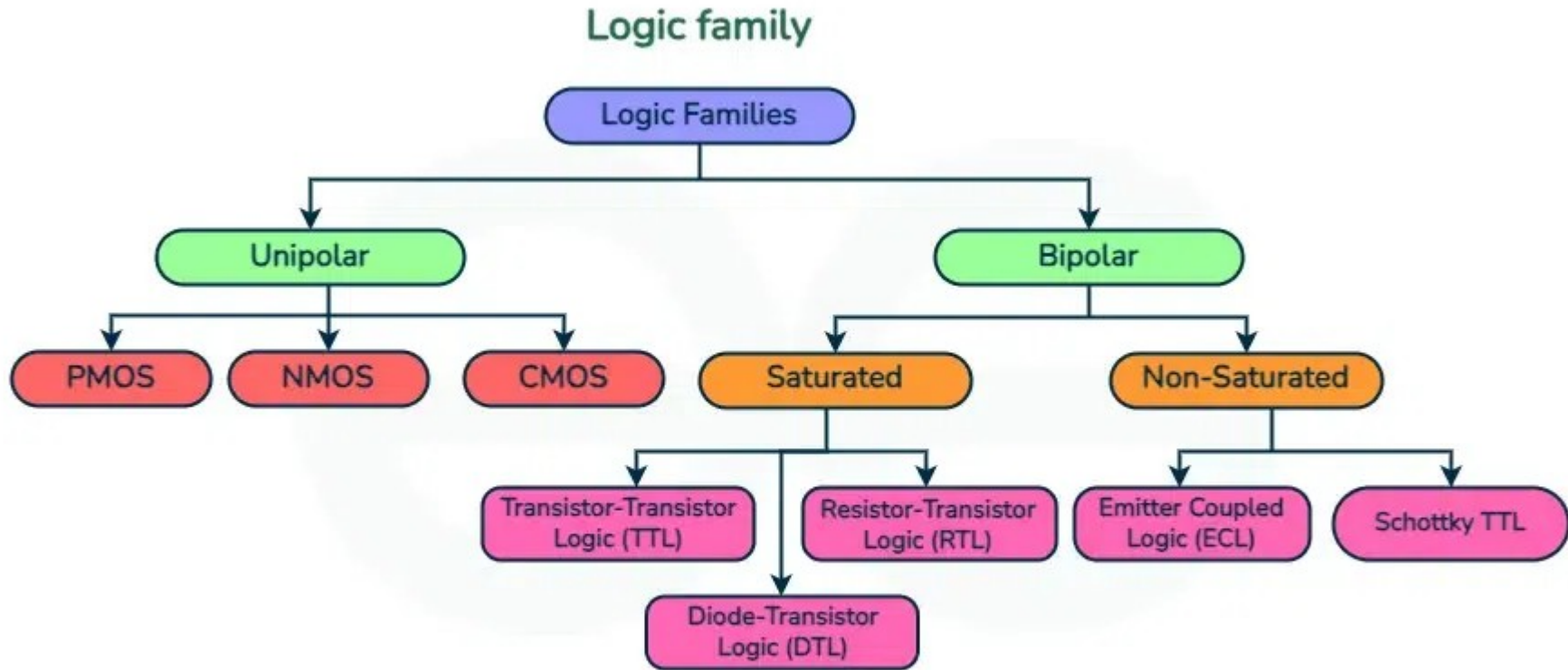


Switching Theory




Akira Nakashima from Japan (1936)

Claude Shannon from US (1938)

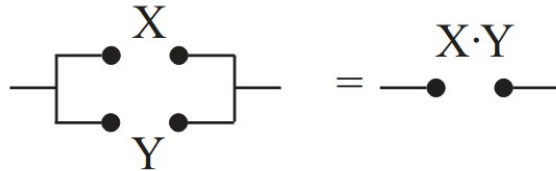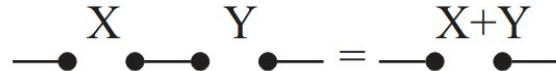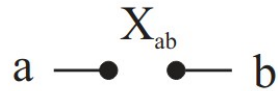Victor Sheshtakov from Soviet Union (1938 Ph.D. Thesis published in 1941)



Shannon

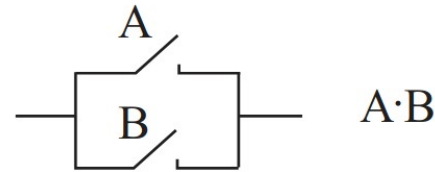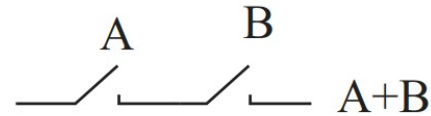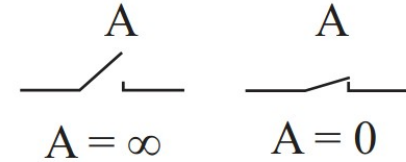


Nakashima

Logic Circuits

Decoder
Multiplexer
ROM
PLA
FPGA
Etc.

Two Input AND Gate

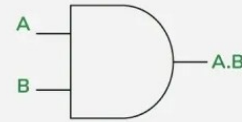

Truth Table

A (Input 1)	B (Input 2)	X = (A.B)
0	0	0
0	1	0
1	0	0
1	1	1

Two Input NAND Gate




Truth Table



Input A	Input B	X = (A.B)'
0	0	1
0	1	1
1	0	1
1	1	0

Sequential Circuits

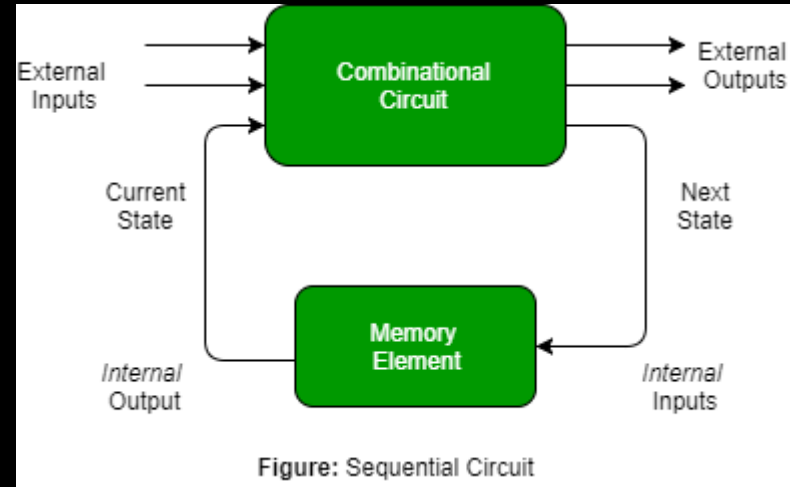
Synchronous vs. Asynchronous
Flip-flop
Latch
Counter
Shift Register
Finite-state machine
Etc.




Algorithmic State Machine charts

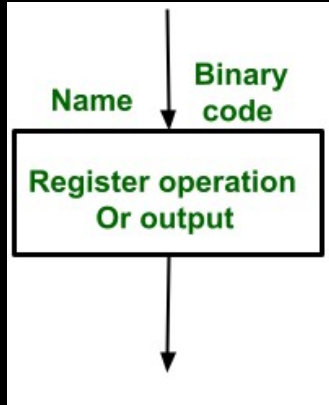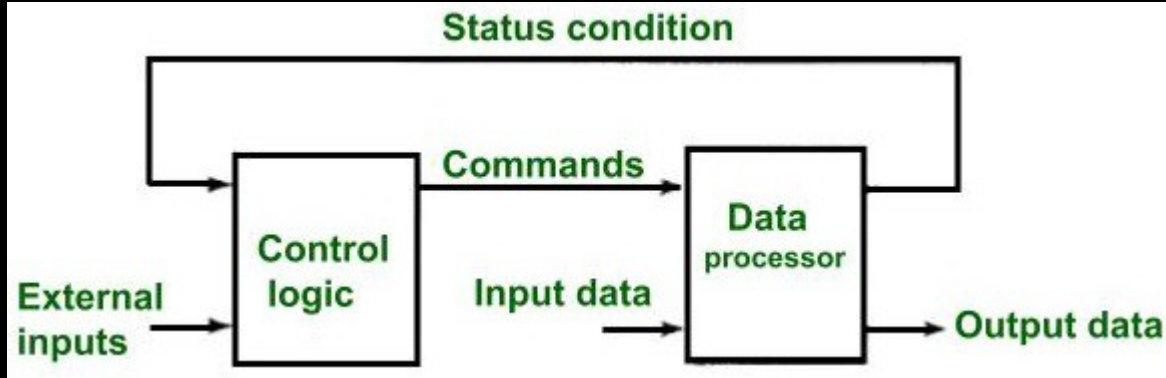

State box

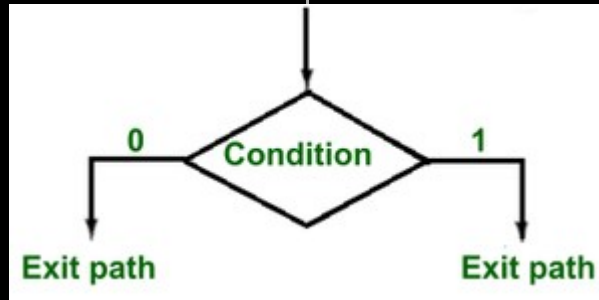

Decision box

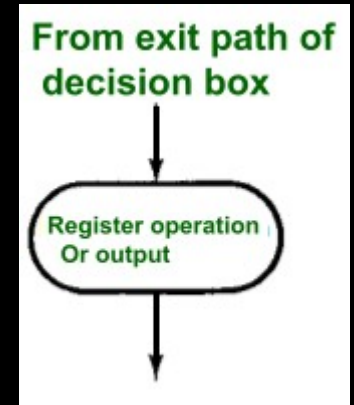

Conditional o/p box