

# Switching Circuit & Logic Design

Lecture 10 : Karnaugh Map for four variables

# Karnaugh Map For Three Variables

AB\CD	00	01	11	10
00	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
01	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>
11	m <sub>12</sub>	m <sub>13</sub>	m <sub>15</sub>	m <sub>14</sub>
10	m <sub>8</sub>	m <sub>9</sub>	m <sub>11</sub>	m <sub>10</sub>

# Max and minterms for four variables

Maxterm	Minterm	A	B	C	D
$M0 = A+B+C+D$	$m0 = A'B'C'D'$	0	0	0	0
$M1 = A+B+C+D'$	$m1 = A'B'C'D$	0	0	0	1
$M2 = A+B+C'+D$	$m2 = A'B'CD'$	0	0	1	0
$M3 = A+B+C'+D'$	$m3 = A'B'CD$	0	0	1	1
$M4 = A+B'+C+D$	$m4 = A'BC'D'$	0	1	0	0
$M5 = A+B'+C+D'$	$m5 = A'BC'D$	0	1	0	1
$M6 = A+B'+C'+D$	$m6 = A'BCD'$	0	1	1	0
$M7 = A+B'+C'+D'$	$m7 = A'BCD$	0	1	1	1
$M8 = A'+B+C+D$	$m8 = AB'C'D'$	1	0	0	0
$M9 = A'+B+C+D'$	$m9 = AB'C'D$	1	0	0	1
$M10 = A'+B+C'+D$	$m10 = AB'CD'$	1	0	1	0
$M11 = A'+B+C'+D'$	$m11 = AB'CD$	1	0	1	1
$M12 = A'+B'+C+D$	$m12 = ABC'D'$	1	1	0	0
$M13 = A'+B'+C+D'$	$m13 = ABC'D$	1	1	0	1
$M14 = A'+B'+C'+D$	$m14 = ABCD'$	1	1	1	0
$M15 = A'+B'+C'+D'$	$m15 = ABCD$	1	1	1	1

# Practice

$$F = A'B'CD + AB'CD' + A'BC'D + ABC'D' + ABCD'$$

# Practice

$$F = (A+B+C+D) (A'+B+C'+D') (A'+B'+C'+D) (A+B'+C'+D') (A'+B'+C+D)$$

# Reduce

AB\CD	00	01	11	10
00				
01				
11				
10				

# Reduce

$$F = \sum_m (2, 3, 6, 7, 8, 10, 11, 13, 14)$$

# Reduce

$$F = \prod_M (4, 6, 11, 14, 15)$$