 


Switching Circuit & Logic Design

Lecture 3 : DTL, TTL




Things to cover


- DTL – NAND and NOR
- TTL – NAND and NOR

Book : Fundamentals of Digital Circuits, A. Anand Kumar


Diode-transistor Logic

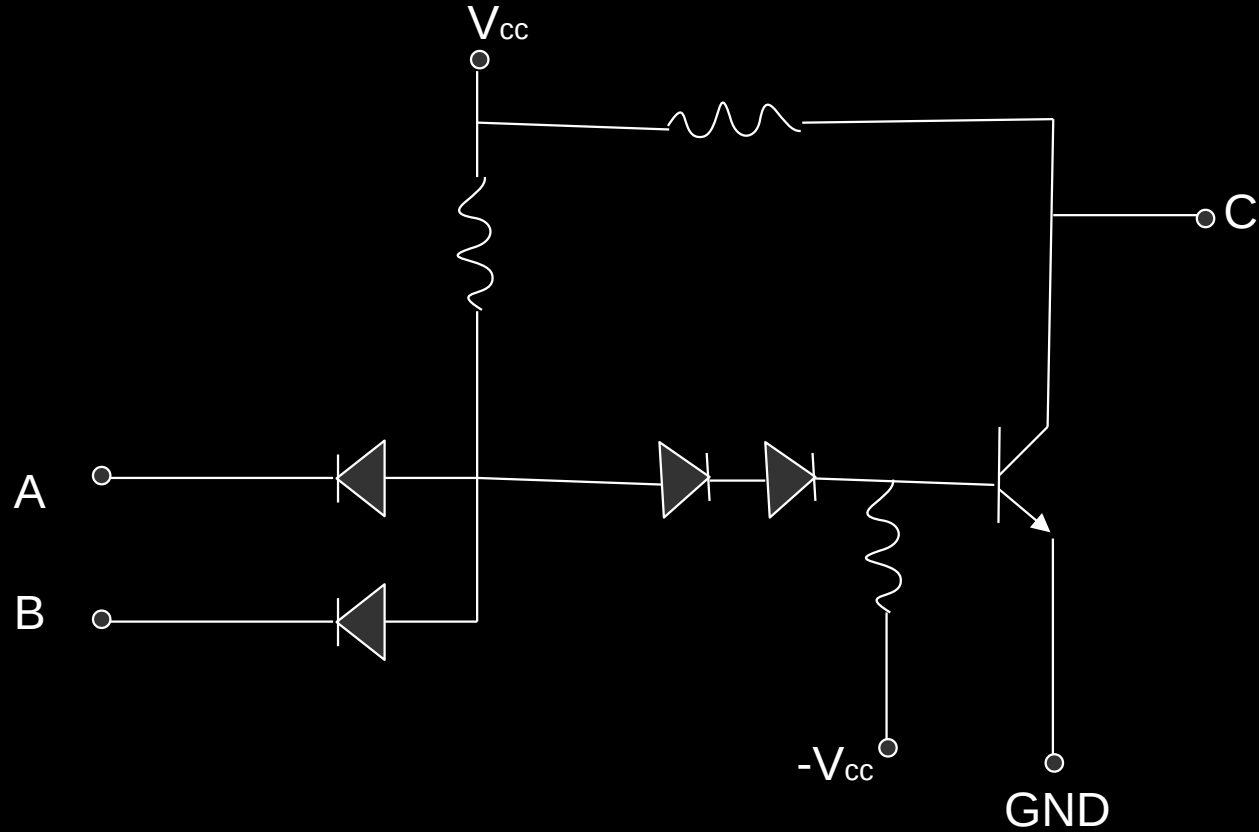

Diode-transistor Logic

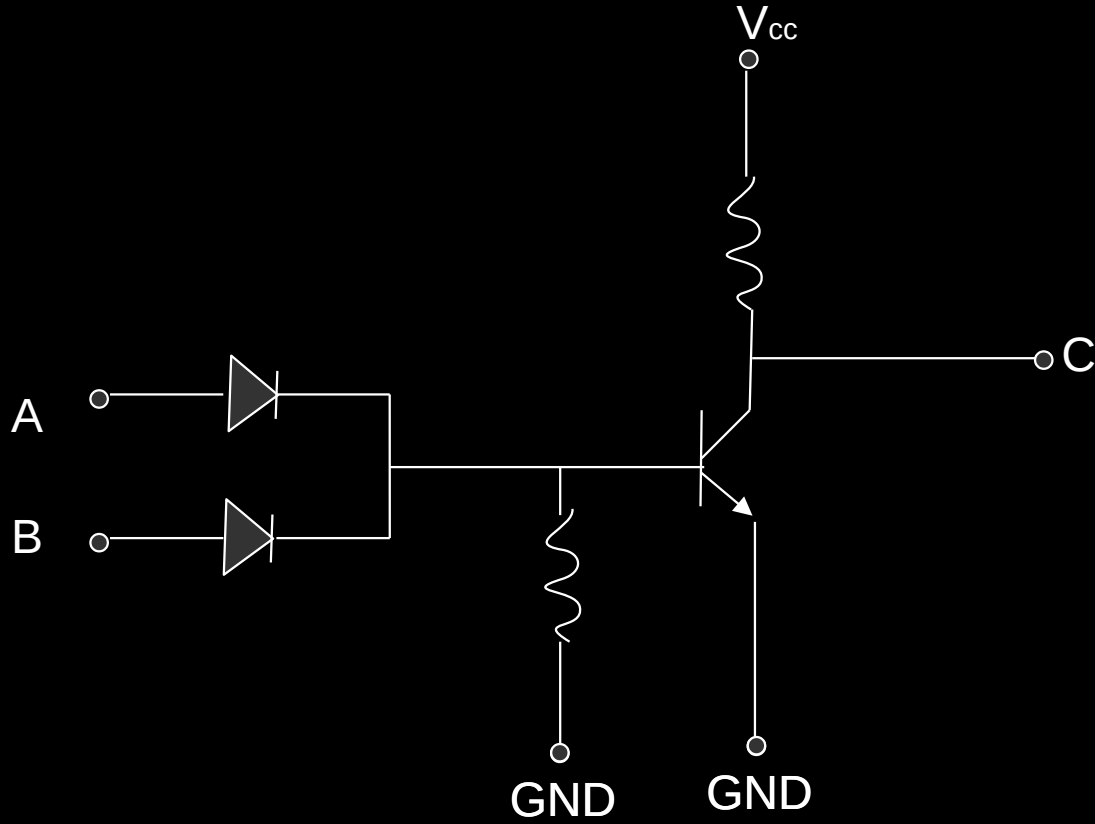

Transistor-transistor Logic

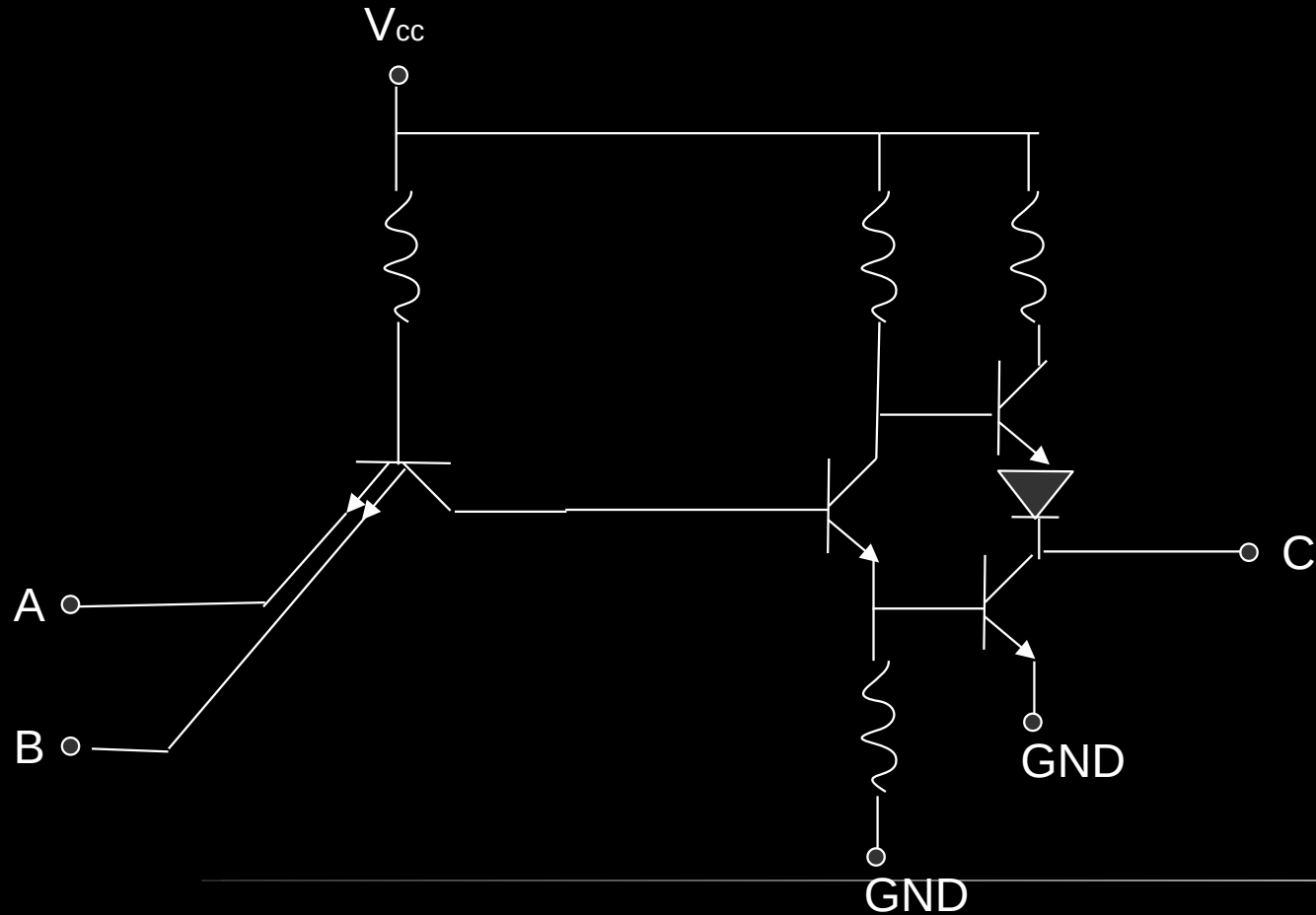

Transistor-transistor Logic

