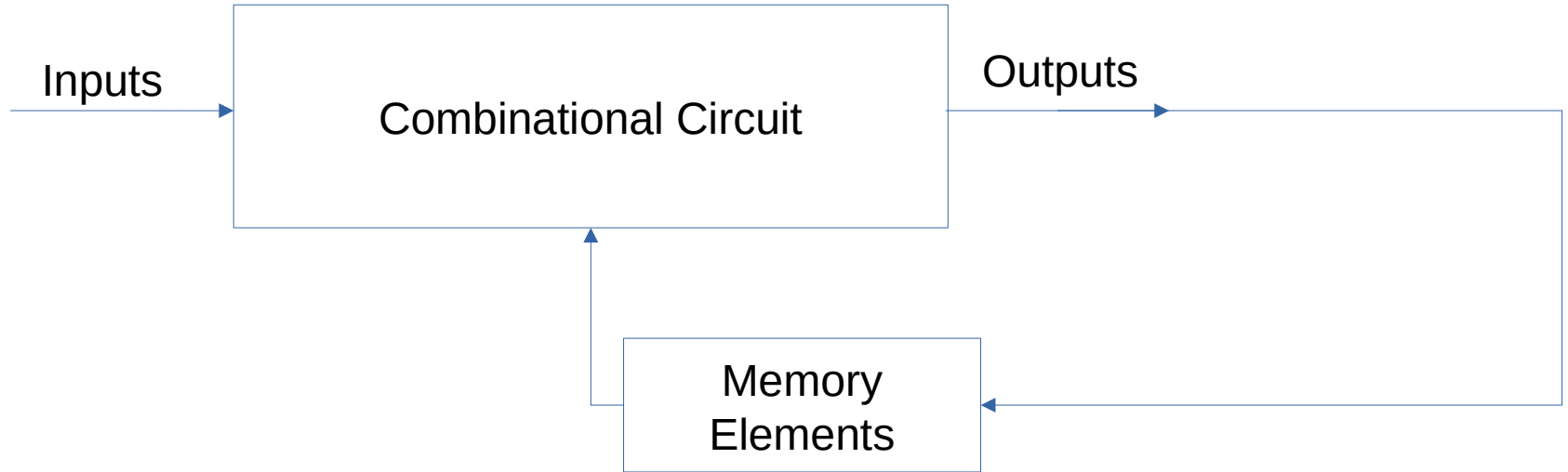
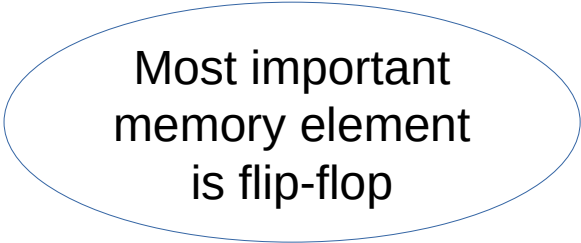

Switching Circuit & Logic Design

Lecture 20 :
Synchronous Circuit

Synchronous Circuit




Latches and Flip-Flops




Most important
memory element
is flip-flop

Latches and Flip-Flops

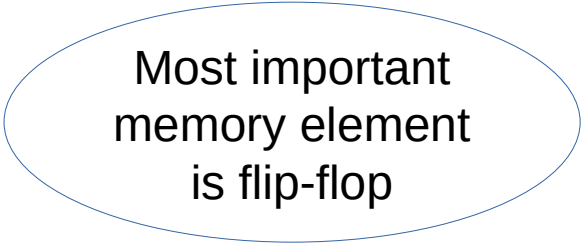

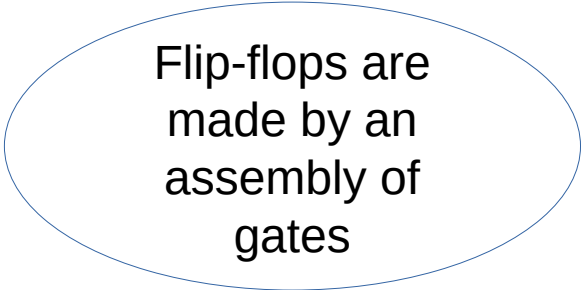Most important
memory element
is flip-flop



Flip-flops are
made by an
assembly of
gates

Latches and Flip-Flops

Most important
memory element
is flip-flop

Flip-flops are
made by an
assembly of
gates

Flip-flop has
only “TWO”
outputs

Q →

Q' →

Latches and Flip-Flops

Most important
memory element
is flip-flop

Flip-flops are
made by an
assembly of
gates

Flip-flop has
only “TWO”
outputs



Q →

Q' →

Flip-flop has
only “TWO”
stable states


→ “ONE” bit
memory

S-R latch

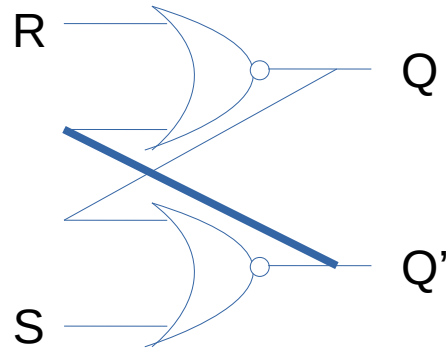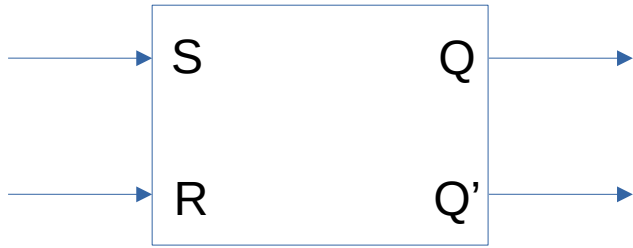


S	R	Q_n	Q_{n+1}	State
0	0	0	0	No Change
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	x	Indeterminate/Invalid
1	1	1	x	

S-R Latch with NAND

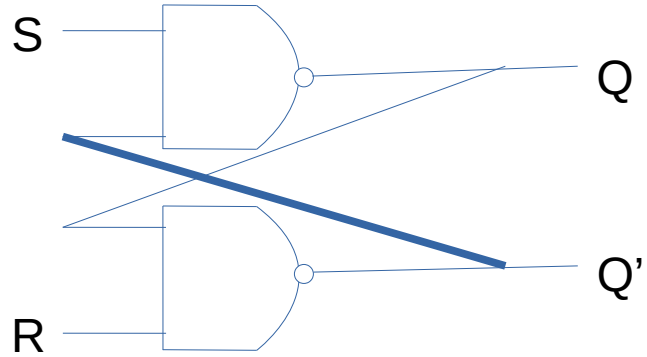

Flip-Flop

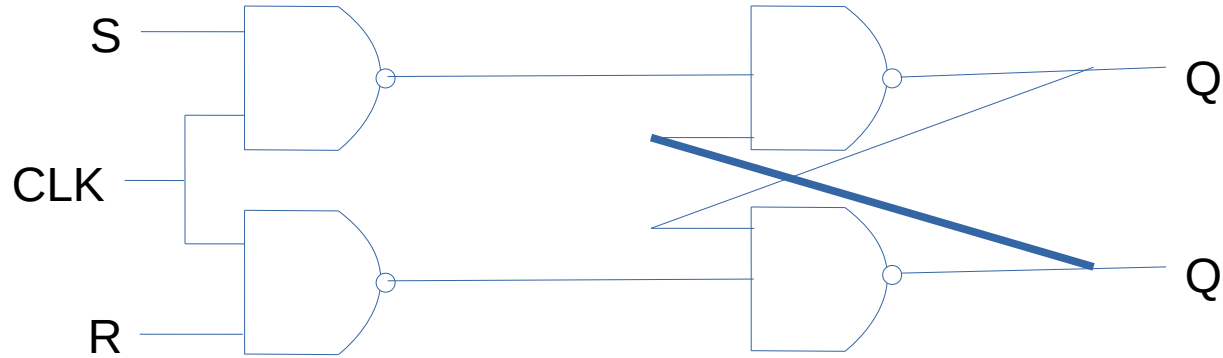

clk	S	R	Q_n	Q_{n+1}	State
1	0	0	0	0	No Change
1	0	0	1	1	
1	0	1	0	0	Reset
1	0	1	1	0	
1	1	0	0	1	Set
1	1	0	1	1	
1	1	1	0	x	Indeterminate/ Invalid
1	1	1	1	x	
0	x	x	0	0	No Change
0	x	x	1	1	