 



# Switching Circuit & Logic Design

Lecture 10 : Karnaugh Map for three variables



# Max and minterms for three variables


Maxterm	Minterm	A	B	C
$M_0 = A+B+C$	$m_0 = A'B'C'$	0	0	0
$M_1 = A+B+C'$	$m_1 = A'B'C$	0	0	1
$M_2 = A+B'+C$	$m_2 = A'BC'$	0	1	0
$M_3 = A+B'+C'$	$m_3 = A'BC$	0	1	1
$M_4 = A'+B+C$	$m_4 = AB'C'$	1	0	0
$M_5 = A'+B+C'$	$m_5 = AB'C$	1	0	1
$M_6 = A'+B'+C$	$m_6 = ABC'$	1	1	0
$M_7 = A'+B'+C'$	$m_7 = ABC$	1	1	1

 

# Karnaugh Map For Three Variables


A\BC	00	01	11	10
0	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
1	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>

A\BC	00	01	11	10
0	M <sub>0</sub>	M <sub>1</sub>	M <sub>3</sub>	M <sub>2</sub>
1	M <sub>4</sub>	M <sub>5</sub>	M <sub>7</sub>	M <sub>6</sub>

 

 
# Practice

$$F = A'B'C + AB'C + A'BC' + ABC' + ABC$$


 
# Practice

$$F = (A+B+C) (A'+B+C') (A'+B'+C') (A+B'+C') (A'+B'+C)$$




# Reduce

A\BC	00	01	11	10
0				
1				



# Reduce

$$F = \sum_m (0, 2, 3, 4, 5, 6)$$

 

# Reduce


$$F = \prod_M (0,1,2,3,4,7)$$

---





# Design the following logic circuit

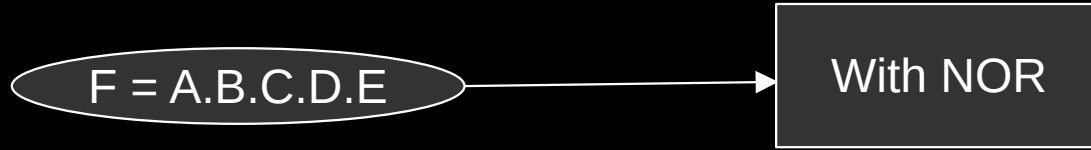

# Design the following logic circuit

