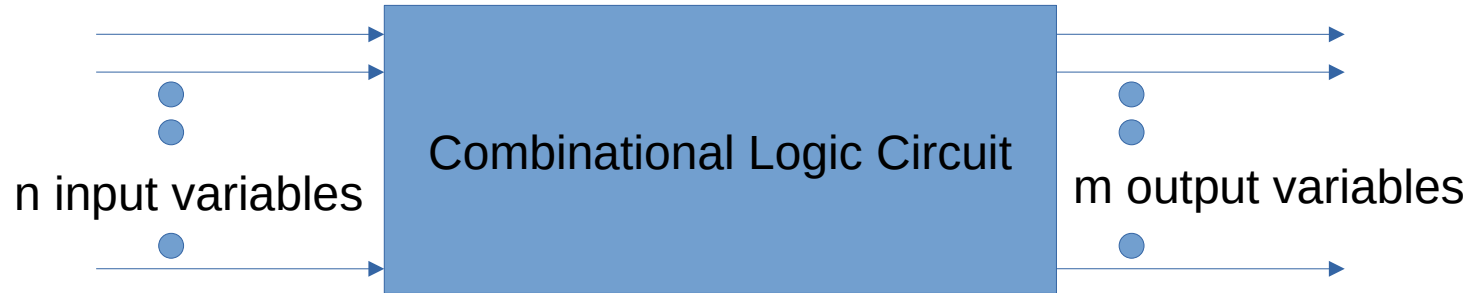

Switching Circuit & Logic Design

Lecture 16 : Combinational Circuit

Content

- What is combinational Logic Design
 - Half Adder
 - Full Adder
 - Parallel Adder
 - Adder / Subtractor
-

Combinational Circuit




Half Adder

Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Full Adder

Inputs			Sum	Carry out
A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Binary Parallel Adder

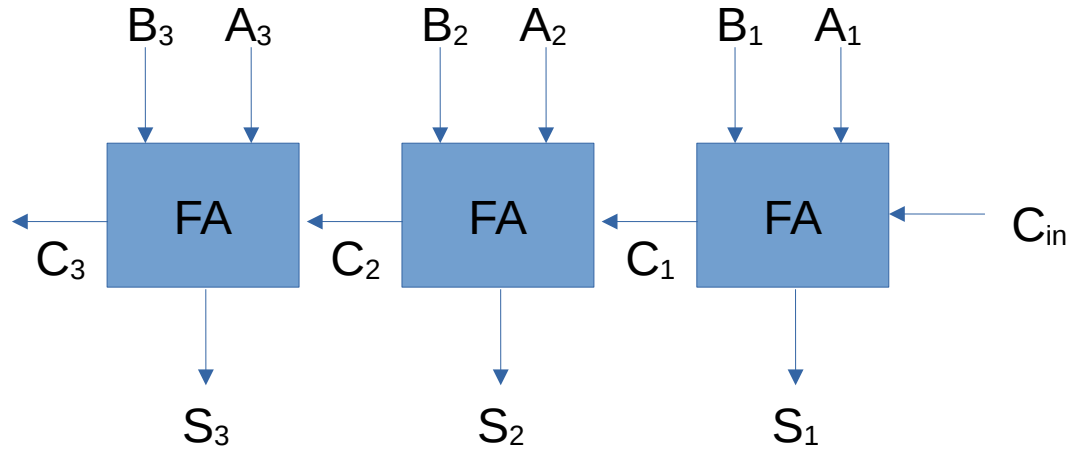

Adder / Subtractor

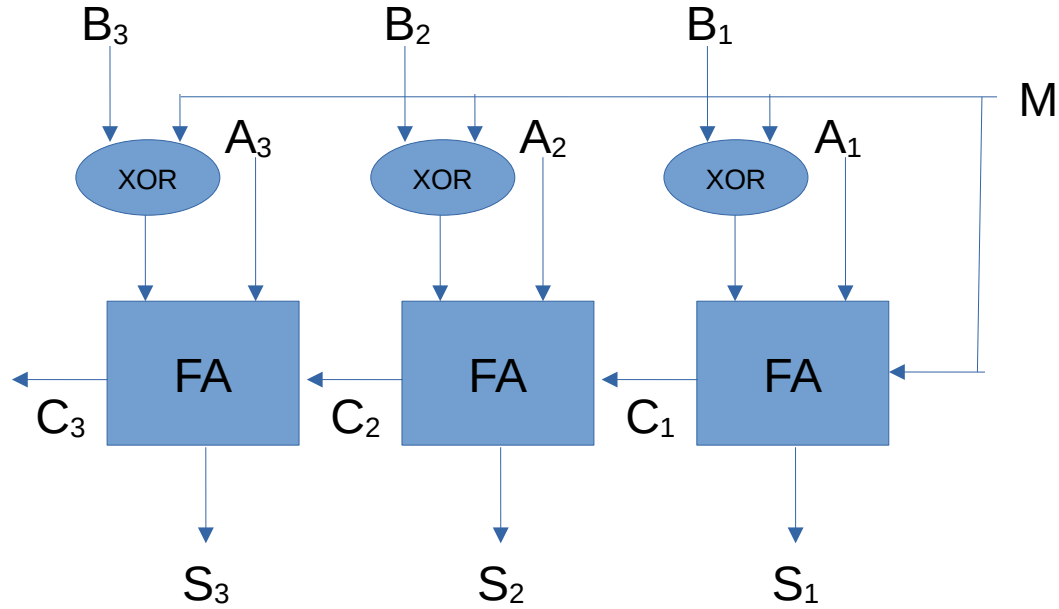

Subtractor

$$A \text{ XOR } 1 = A'$$

1's Complement  B'

$$A \text{ XOR } 0 = A$$

2's Complement  +1
