 


Switching Circuit & Logic Design

Lecture 7 : Logic Gates & Boolean Algebra



Things to cover

- LOGIC GATES
 - Basic Gates
 - Universal Gates
 - XOR, XNOR

Book : Fundamentals of Digital Circuits, A. Anand Kumar

Prove the following

$$A + BC = (A+B).(A+C)$$

$$A + B = AB + A'B + AB'$$

Prove the following

$$A + BC = (A+B).(A+C)$$



Dual of first Distributive Law

$$\begin{aligned}(A+B).(A+C) &= AA + AC + BA + BC \\ &= A + AC + BA + BC \\ &= A.1 + AC + BA + BC \\ &= A(1+C) + BA + BC \\ &= A.1 + BA + BC \\ &= A.1 + AB + BC \\ &= A(1+B) + BC \\ &= A.1 + BC \\ &= A + BC\end{aligned}$$

//Distributive Law

//Idempotence Law

//Identity

//Distributive

//Dominance

//Commutative

//Distributive

//Dominance




//Identity

Prove the following


$$A + B = AB + A'B + AB'$$

$$\begin{aligned} AB + A'B + AB' &= BA + BA' + AB' && // \text{Commutative Law} \\ &= B(A + A') + AB' && // \text{Distributive Law} \\ &= B.1 + AB' && // \text{Complementary Law} \\ &= B + AB' && // \text{Idempotent Law} \\ &= (B+A).(B+B') && // \text{Distributive Law} \\ &= (B+A).1 && // \text{Complementary Law} \\ &= B+A && // \text{Idempotent Law} \\ &= A+B && // \text{Commutative Law} \end{aligned}$$




Basic Gates

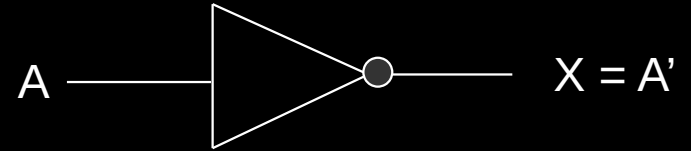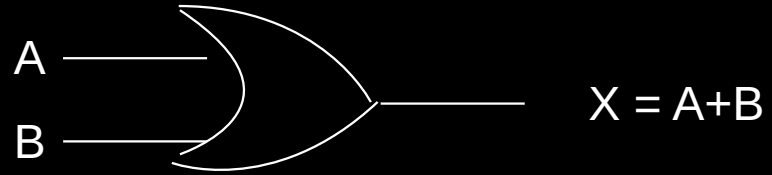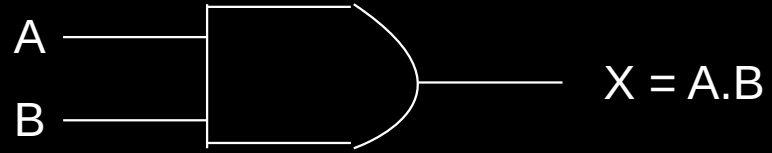


Universal Gates -- NAND

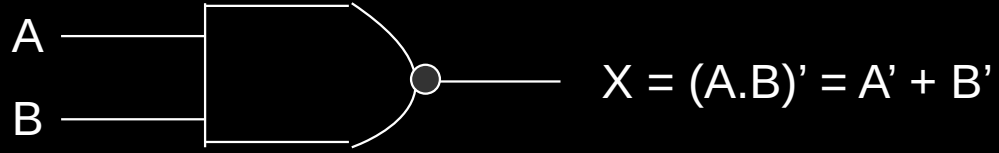


Universal Gates -- NAND

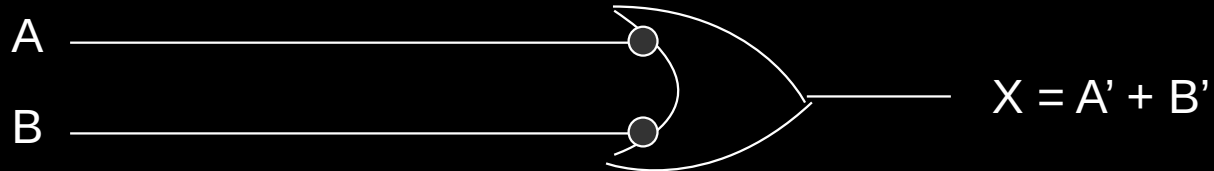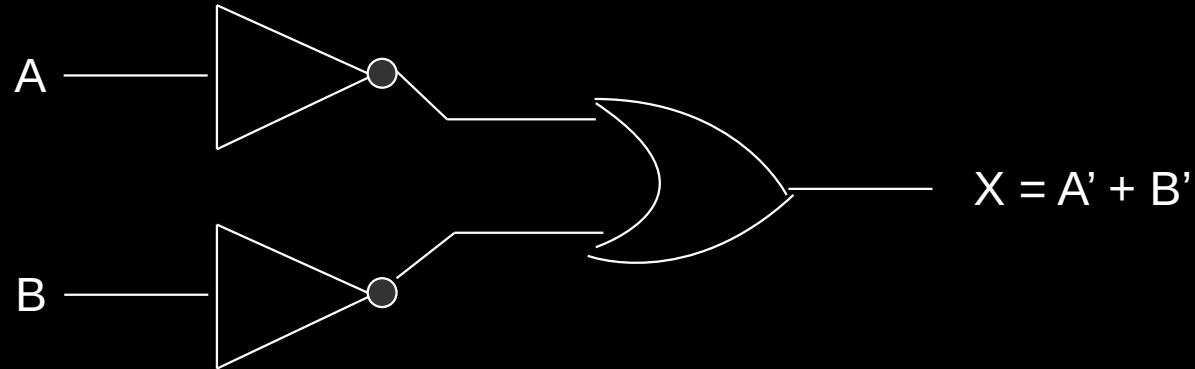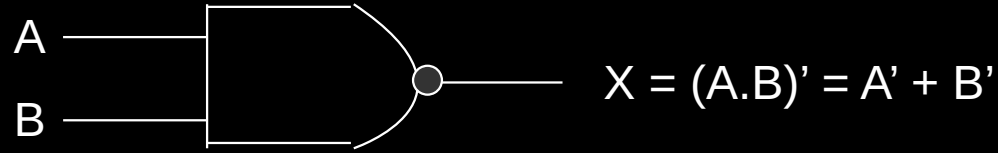


Implement Inverter

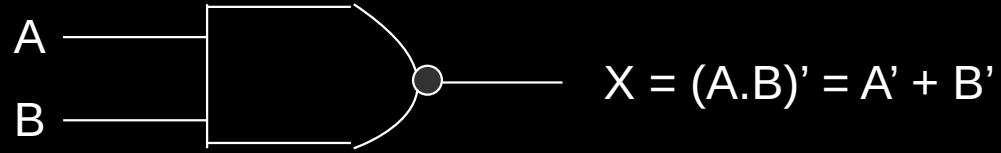

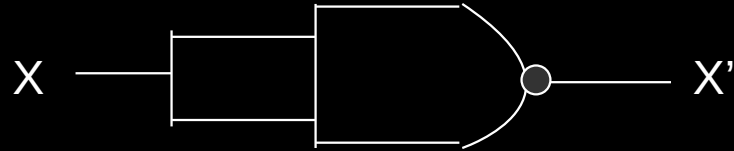
If $A = B$, $\Rightarrow X = (A.A)' = A'$





Implement AND, OR Gates

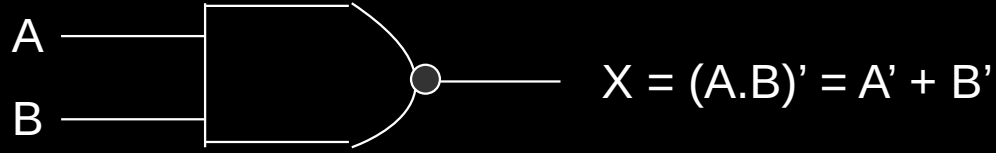


Universal Gates -- NOR

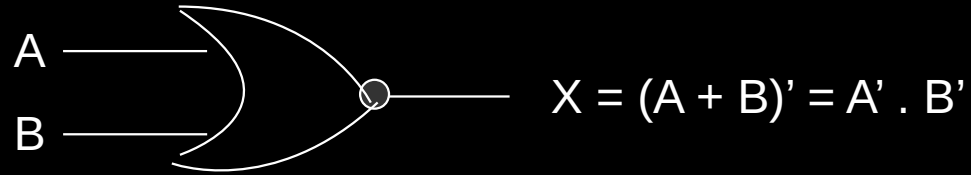


Universal Gates -- NOR

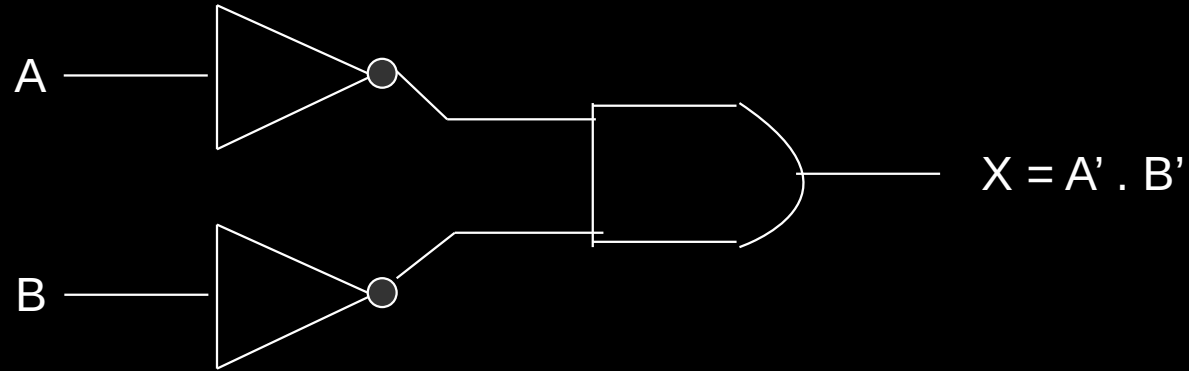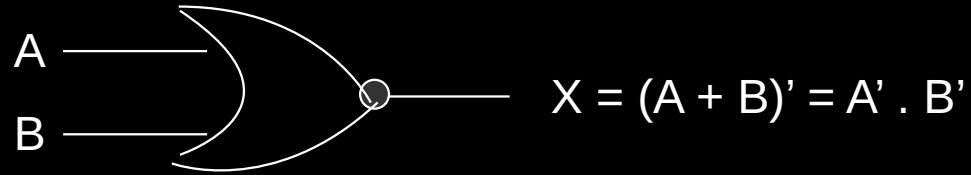


Implement NOT

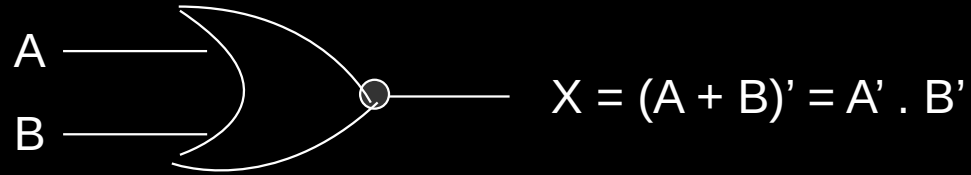


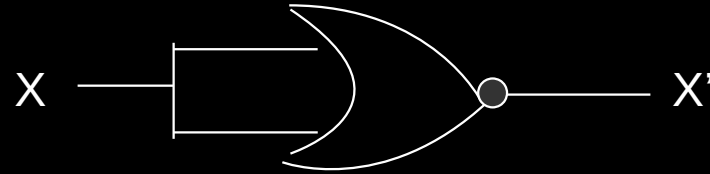
If $A = B$, $\Rightarrow X = (A + A)' = A'$




Implement AND, OR Gates

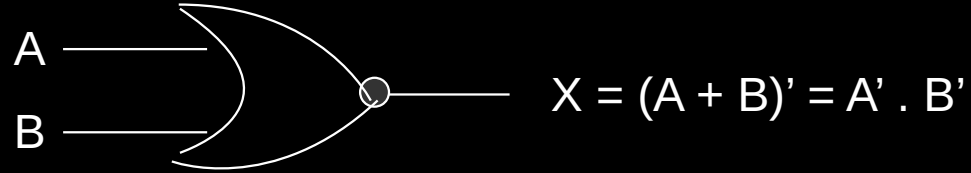

XOR, XNOR Gate

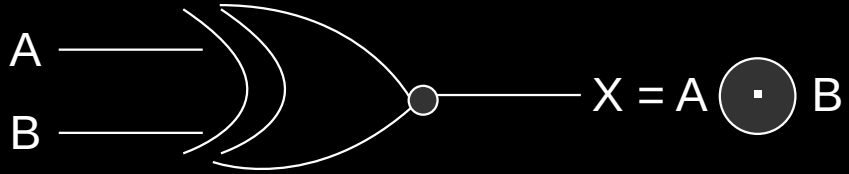
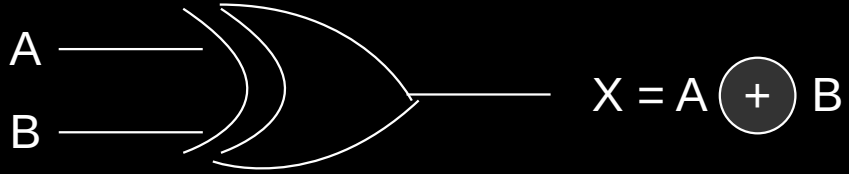


XOR Gate

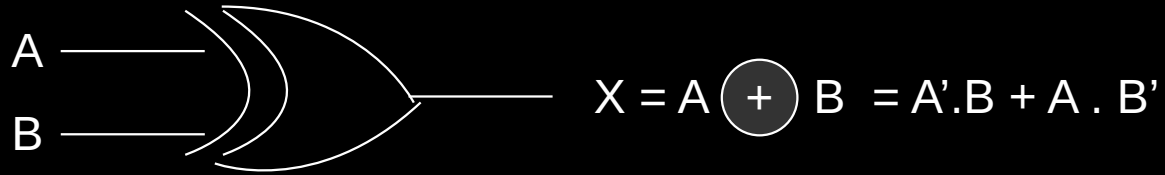


A	B	$X = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

XOR Gate

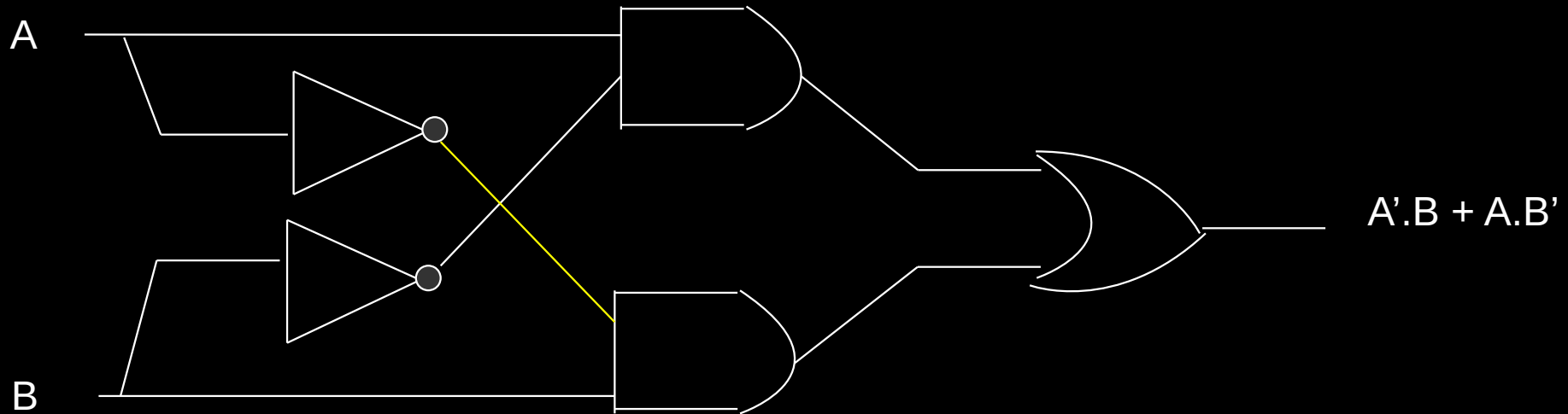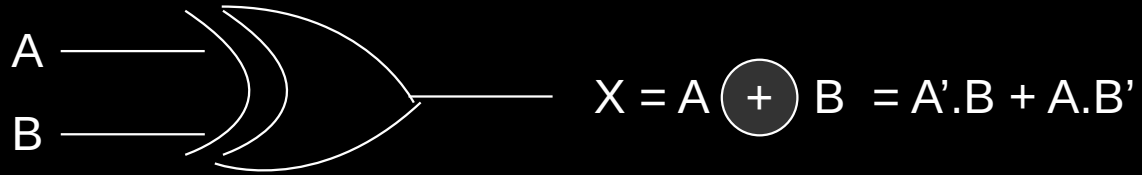

XNOR Gate

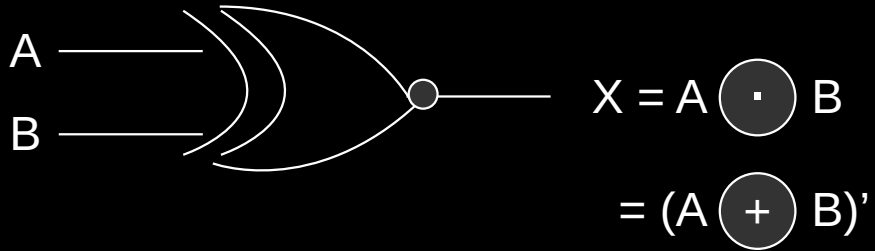

A	B	$X = A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

XNOR Gate

